

Combinational Logic Circuits

Sum of products Method

A	B	fundamental products
0	0	$\bar{A}\bar{B}$
0	1	$\bar{A}B$
1	0	$A\bar{B}$
1	1	AB

The fundamental products are also called minterms.
 minterms are represented as m_i where i is the decimal equivalent of binary value.

$$m_0 \rightarrow \bar{A}\bar{B} \quad \text{two bit input}$$

$$m_0 \rightarrow \bar{A}\bar{B}\bar{C} \quad \text{three bit input}$$

If $f=1$, we should consider that minterm which is defining the function f .

Example $y = \bar{A}BC + A\bar{B}C + ABC$


$$= m_3 + m_5 + m_6$$

$$y = f(A, B, C) = \sum_m (3, 5, 6)$$

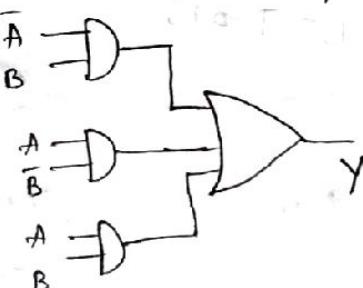Example

$$\begin{array}{ccc} A & B & Y \\ 0 & 0 & 0 \end{array} \quad y = \bar{A}\bar{B} + A\bar{B} + AB$$

$$\begin{array}{ccc} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 1 \end{array} \quad y = f(A, B) = \sum_m (1, 2, 3)$$



Karnaugh Map

2 variables

	0	1
0		
1		

	0	1
00		
01		
11		
10		

3 variables

	00	01	11	10
0				
1				

Steps:

- Representation
- Grouping
- Adjacency
- overlapping zone

4 variables

	00	01	11	10
00				
01				
11				
10				

\bar{A}	\bar{A}
A	A

(a) 1-Variable map

A	B	\bar{B}	B
	$\bar{A}\bar{B}$	$\bar{A}B$	1
A	$A\bar{B}$	AB	3
	2	3	

(b) 2-Variable map

A	BC	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
	$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}C$	$\bar{A}B\bar{C}$	$A\bar{B}C$	$A\bar{B}\bar{C}$
A	0	1	3	2	
	4	5	7	6	

(c) 3-Variable map

AB	CD	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
	$\bar{A}\bar{B}$	$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}\bar{B}\bar{C}D$	$\bar{A}\bar{B}CD$	$\bar{A}\bar{B}C\bar{D}$
$\bar{A}B$	0	1	3	2	
	4	5	7	6	
AB	$A\bar{B}\bar{C}\bar{D}$	$A\bar{B}\bar{C}D$	$A\bar{B}CD$	$A\bar{B}C\bar{D}$	
	12	13	15	14	
$A\bar{B}$	$A\bar{B}\bar{C}\bar{D}$	$A\bar{B}\bar{C}D$	$A\bar{B}CD$	$A\bar{B}C\bar{D}$	
	8	9	11	10	

(d) 4-Variable map

$$\textcircled{1} \quad f(a,b) = \sum_m(0,2)$$

	0	1
0	1	0
1	1	0

$$Y = \bar{B}$$

$$f(a,b) = \sum_m(0)$$

	0	1
0	1	0
1	0	0

$$Y = \bar{A}\bar{B}$$

$$\textcircled{2} \quad f(A,B,C) = \sum_m(-2,3,4,5)$$

AB	00	01	11	10
	D	D	0	1
AB	1	1	0	0
	1	1	0	0

$$Y = A\bar{B} + \bar{A}B$$

$$\textcircled{3} \quad f(A, B, C, D) = \sum_m (0, 2, 3, 4, 9, 11)$$

	00	01	11	10
00	1	0	1	1
01	1	0	0	0
11	0	0	0	0
10	0	1	1	0

$$Y = \bar{A}\bar{C}\bar{D} + A\bar{B}D + \bar{A}\bar{B}C$$

$$\textcircled{4} \quad f(A, B, C) = \sum_m (0, 1, 4, 5)$$

	00	01	11	10
0	1	1	0	0
1	1	1	0	0

$$Y = \bar{B}$$

$$\textcircled{5} \quad f(ABC) = \sum_m (0, 1, 2, 3, 4, 5, 6, 7)$$

	00	01	11	10
0	1	1	1	1
1	1	1	1	1

$$Y = 1$$

$$\textcircled{6} \quad Y = A\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}$$

	00	01	11	10
0	1	1	1	0
1	1	1	0	0

$$Y = \bar{A}C + \bar{B}$$

$$\textcircled{7} \quad f(ABCD) = \sum_m (2, 4, 5, 9, 12, 13)$$

	00	01	11	10
00	0	0	0	1
01	1	1	0	0
11	1	1	0	0
10	0	1	0	0

$$Y = \bar{A}\bar{B}C\bar{D} + A\bar{C}D + BC$$

$$⑧ f(A,B,C,D) = \sum m(0, 2, 3, 8, 10, 11, 12, 14)$$

	00	01	11	10
00	1	0	1	1
01	0	0	0	0
11	1	0	0	1
10	1	0	1	1

prime implicants

$\bar{A}D$

$\bar{B}C$

$A\bar{D}$

$$⑨ f(A,B,C,D) = \sum m(1, 5, 6, 7, 11, 12, 13, 15)$$

	00	01	11	10
00	0	1	0 0	
01	0	1	1 1	
11	1 1	1	0	
10	0 0	1	0	

prime implicants

essential PI

ABC

ABC

ACD

ACD

$\bar{A}BC$

$\bar{A}BC$

$\bar{A}\bar{C}D$

$\bar{A}\bar{C}D$

BD

-

$$⑩ f(A,B,C,D) = \sum m(1, 2, 3, 5, 6, 7, 11, 12, 13, 14, 15)$$

	00	01	11	10
00	0	1 1 1		
01	0	1 1 1		
11	1 1 1	1 1 1		
10	0 0 1	1	0	

prime Implicants

EPI

AB

AB

CD

CD

$\bar{A}D$

$\bar{A}D$

$\bar{A}C$

$\bar{A}C$

BD

-

BC

-

$$\textcircled{11} \quad f(A, B, C, D) = \sum_m (7, 9, 10, 11, 12, 13, 14, 15)$$

	00	01	11	10	PI	EPI
00	0	0	0	0	AB	AB
01	0	0	1	0	AC	BCD
11	1	1	1	1	AD	AD
10	0	1	1	1	BCD	AC

$$\textcircled{12} \quad \neg f(A, B, C, D) = \sum_m (0, 1, 2, 3, 4, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$Y = \overline{ABC} + AD + \overline{BD} + \overline{CD} + \overline{AC} + \overline{AB}$$

	00	01	11	10	PI
00	1	1	1	1	A
01	1	0	1	1	C
11	1	1	1	1	B
10	1	1	1	1	D

$$\textcircled{13} \quad f(ABCD) = \sum_m (5, 7, 8, 12)$$

	00	01	11	10	PI
00	0	0	0	0	
01	0	1	1	0	\overline{ABC}
11	1	0	0	0	$\overline{A}\overline{B}\overline{D}$
10	1	0	0	0	

$$\textcircled{14} \quad \neg f(abcd) = \sum_m (0, 3, 4, 5, 7, 9, 13, 14, 15)$$

	00	01	11	10	PI \rightarrow	EPI \rightarrow
00	1	0	1	0	$BD, \overline{A}\overline{C}\overline{D}, \overline{ABC}, \overline{ACD}$	
01	1	1	1	0		$ABC, A\overline{C}D$
11	0	1	1	1		
10	0	1	0	0		$\overline{A}\overline{C}D, \overline{ABC}, \overline{A}CD, ABC, \overline{A}\overline{C}D$

Don't Care Condition

$$\textcircled{1} \quad f(a,b,c,d) = \sum_m(0,2,5,7,8,10,13,15) + \sum_d(1,4,11,14)$$

	00	01	11	10	PI	EPI
00	1	x	0	1	$\bar{a}\bar{c}$	-
01	x	1	1	0	$b\bar{d}$	$b\bar{d}$
11	0	1	1	x	$a\bar{c}$	-
10	1	0	x	1	$\bar{b}\bar{d}$	$\bar{b}\bar{d}$

$$\textcircled{2} \quad f(a,b,c,d) = \sum_m(1,3,5,7,8,10,12,13,14) + \sum_d(4,6,15)$$

	00	01	11	10	PI
00	0	1	1	0	$\bar{A}D$
01	x	1	1	x	B
11	1	1	x	1	$A\bar{D}$
10	1	0	0	1	-

$$\textcircled{3} \quad f(a,b,c,d) = \sum_m(6,7,9,10,13) + \sum_d(1,4,5,11,15)$$

	00	01	11	10	P.I	EPI	or
00	0	x	0	0	$\bar{A}B$	$\bar{A}B$	$\bar{A}B$
01	x	x	1	1	$\bar{C}D$	-	$\bar{C}D$
11	0	1	x	0	$\bar{A}D$	AD	-
10	0	1	x	1	$A\bar{B}C$	$A\bar{B}C$	$A\bar{B}C$

$$\textcircled{4} \quad f(a,b,c,d) = \sum_m(0,1,3,7,8,12) + \sum_d(5,10,13,14)$$

	00	01	11	10	PI
00	1	1	1	0	$\bar{A}\bar{B}\bar{C}$
01	0	x	1	0	$\bar{A}D$
11	1	x	0	x	-
10	1	0	0	x	$A\bar{D}$

$$④ f(a,b,c,d) = \overline{a}\overline{c}d + \overline{a}cd + \overline{b}\overline{c}d + ab\overline{c} + \overline{a}b\overline{c}d$$

	00	01	11	10	PI	EPI
00	1	1	1	1	$\overline{a}b$	-
01	0	1	1	0	$\overline{a}d$	$\overline{a}d$
11	0	0	0	0	$\overline{b}c$	$\overline{b}c$
10	1	0	1	1	$\overline{b}d$	$\overline{b}d$

$$⑤ f(a,b,c,d) = \Sigma(0,1,2,5,8,15) + \Sigma_d(6,9,10)$$

	00	01	11	10	PI	EPI
00	1	1	0	1	$\overline{a}cd$	$\overline{a}cd$
01	0	1	x	x	$\overline{b}\overline{d}$	$\overline{b}\overline{d}$
11	0	0	1	0	bcd	bcd
10	1	0	0	x	\overline{acd}	-

$$⑥ f(a,b,c,d) = \Sigma(7,9,11,12,13,14) + \Sigma_d(3,5,6,15)$$

	00	01	11	10	PI	EPI
00	0	0	x	0	bc	bc
01	0	x	1	x	ad	ad
11	1	1	x	1	$a\overline{b}\overline{c}$	$a\overline{b}\overline{c}$
10	0	1	1	0	\overline{bd}	-

$$⑦ f(a,b,c,d) = \Sigma(7,9,12,13,14,15) + \Sigma_d(4,11)$$

	00	01	11	10	PI	EPI
00	0	0	0	0	ab	ab
01	+	0	1	0	ad	ad
11	1	1	1	1	bcd	bcd
10	0	1	x	0	$b\overline{c}\overline{d}$	-

Product of Sums Methods

A B fundamental products

$$0\ 0 \quad A+B$$

$$0\ 1 \quad A+\bar{B}$$

$$1\ 0 \quad \bar{A}+B$$

$$1\ 1 \quad \bar{A}+\bar{B}$$

$M_i \rightarrow$ maxterms, i is the decimal equivalent of binary values

$$M_0 \rightarrow A+B \quad \text{two bit mps}$$

$$M_0 \rightarrow A+B+C \quad \text{three bit mps}$$


$$y = (A+\bar{B}+\bar{C}) (\bar{A}+B+\bar{C}) (\bar{A}+\bar{B}+C)$$

$$y = \bar{f}(ABC) = \prod_M (3, 5, 6)$$

Example

A	B	y
0	0	0
0	1	1
1	0	1
1	1	1
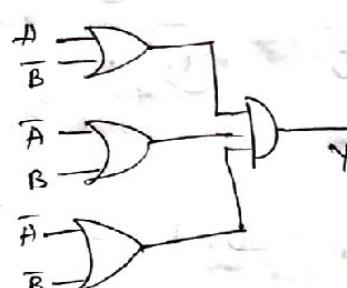
$$y = (\bar{A}+\bar{B}) (\bar{A}+B) (\bar{A}+\bar{B})$$



$$y = \bar{f}(A,B) = \prod_M (0)$$

$$\textcircled{1} \quad f(abc) = \prod_M (3, 4, 5, 7)$$

	00	01	11	10	PI	EPI
0	1	1	0	1	$\bar{A}+B$	$\bar{A}+B$
1	0	0	0	1	$\bar{B}+\bar{C}$	$\bar{B}+\bar{C}$

$$\begin{array}{l} \text{PI} \\ \bar{A}+B \\ \bar{B}+\bar{C} \\ \bar{A}+\bar{C} \end{array}$$

$$\textcircled{2} \quad f(abc) = \prod_M (0, 1, 4, 6)$$

	00	01	11	10	PI	EPI
0	0	0	1	1	$A+B$	$A+B$
1	0	1	1	0	$B+C$	-

$$\begin{array}{l} \text{PI} \\ A+B \\ B+C \\ \bar{A}+C \end{array}$$

$$f(a,b,c,d) = \prod_N (0, 2, 3, 8, 9, 10, 12, 14)$$

	00	01	11	10
00	0	1	0	0
01	1	1	1	0
11	0	1	1	0
10	0	0	1	0

PI

$$\bar{A} + D$$

$$\bar{A} + B + C$$

$$A + B + \bar{C}$$

$$B + D$$

$$f(a,b,c,d) = \prod_N (1, 3, 6, 9, 11, 14, 15)$$

PI

EPI

	00	01	11	10
00	1	0	0	1
01	1	1	1	0
11	1	1	0	0
10	1	0	0	1

$$B + \bar{D}$$

$$B + \bar{D}$$

$$\bar{A} + \bar{C} + \bar{D}$$

$$\bar{A} + \bar{C} + \bar{D}$$

$$\bar{B} + \bar{C} + D$$

$$\bar{B} + \bar{C} + D$$

$$\bar{A} + \bar{B} + \bar{C}$$

$$-$$

$$f(a,b,c,d) = \prod_N (0, 1, 3, 8, 9, 10, 14, 15)$$

	00	01	11	10
00	0	0	0	1
01	1	1	1	1
11	1	1	0	0
10	0	0	1	0

PI

$$B + C$$

$$\bar{A} + \bar{B} + \bar{C}$$

$$\bar{A} + \bar{C} + D$$

$$A + B + \bar{D}$$

$$f(a,b,c,d) = \Pi(1,4,5,6,14)$$

	00	01	11	10	<u>PI</u>
00	1	0	1	1	$A + \bar{B} + C$
01	0	0	1	0	$A + C + \bar{D}$
11	1	1	1	-	$\bar{B} + \bar{C} + D$
10	1	1	1	1	

Dont Care Condition

$$f(a,b,c,d) = \Pi_M(0,3,4,5,6,7,11,15) + \Pi_d(2,14)$$

	00	01	11	10	<u>PI</u>
00	0	1	0	-	$A + D$
01	0	0	0	0	$A + \bar{B}$
11	1	1	0	-	$\bar{C} + \bar{D}$
10	1	1	0	1	

$$f(a,b,c,d) = \Pi(0,1,4,5,8,9,11) + \Pi_d(2,10)$$

	00	01	11	10	<u>PI</u>	<u>EPI</u>
00	0	0	1	-	$A + C$	$A + C$
01	0	0	1	1		$\bar{A} + B$
11	1	1	1	1	$b + c$	-
10	0	0	0	-	$b + d$	-

$$f(a,b,c,d) = \Pi(2,8,11,15) + \Pi_d(3,12,14)$$

	00	01	11	10	<u>PI</u>
00	1	1	-0		$a + b + \bar{c}$
01	1	1	1	1	$\bar{a} + c + d$
11	-	1	0	-	$\bar{a} + \bar{c} + \bar{d}$
10	0	1	0	1	

$$f(A, B, C, D) = \prod_M (1, 2, 3, 4, 9, 10) + \prod_D (0, 14, 15)$$

	00	01	11	10	PI
00	-	0	0	0	$A+B$
01	0	1	1	-	$B+C+\bar{D}$
11	1	1	-	-	$A+C+D$
10	1	0	1	0	$\bar{A}+\bar{C}+D$

Quine - McCluskey method (Algorithm) for obtaining prime implicants

- ① Represent each minterm in its 1,0 notation
- ② Write down the minterm in increasing order of their index in one column.
- ③ Draw a line after each set of minterms with same index value.
- ④ Set $i=0$
- ⑤ Pick up each term with index i & $i+1$ to see if they differ in exactly one position. If yes, write the result term which results from the combination in 1,0,- notation in a new column & place a 'v' besides the two terms that combined.
If no, proceed with other pairs until all the pairs with indices i & $i+1$ have been compared
- Now draw a line under the last term in the new list.
- ⑥ Set $i=i+1$, repeat Step 5 until all the terms have been covered.

⑦ Repeat Step 4, 5 and 6 on the new list to form another list.

⑧ Terminate the process when no new lists are formed.

⑨ The prime implicants of the function are all those terms without a ' \checkmark ' besides them.

$$① f(a,b,c) = \sum m(0,2,3,4)$$

a	b	c	
0	0	0	0
0	0	1	0
4	1	0	0
3	0	1	1

(0,2) 0-0 $\bar{a}\bar{c}$
 (0,4) -00 $\bar{b}\bar{c}$
 (2,3) 01- $\bar{a}b$

prime implicants: $\bar{a}\bar{c}$, $\bar{b}\bar{c}$, $\bar{a}b$

Essential prime implicants: $\bar{b}\bar{c}$, $\bar{a}b$

	0	2	3	4
$\bar{a}\bar{c}$	✓		✓	
$\bar{b}\bar{c}$		✓		✓
$\bar{a}b$		✓	✓	✓

$$② f(a,b,c) = \sum m(0,1,2,3)$$

VINUTHA. K M.Tech, Ph.D.
 Assistant Professor
 Dept. of ISE
 BMSIT & M. Yelahanka, Bengaluru 560084

a	b	c	
0	0	0	0
0	0	1	✓
1	0	0	1
2	0	1	0
3	0	1	1

(0,1) 00-✓ $(0,1)(2,3) 0--\bar{a}$
 (0,2) 0-0- $(0,2)(1,3) 0-\bar{a}$
 (1,3) 0-1-
 (2,3) 01-

prime implicants: \bar{a}

$$③ f(a,b,c) = \sum_m (0, 1, 2, 3, 4, 5, 6)$$

	a	b	c			
0	0	0	0	(0,1)	00-	✓
1	0	0	1	(0,2)	0-0	✓
2	0	1	0	(0,4)	-00	✓
4	1	0	0	(1,3)	0-1	✓
3	0	1	1	(1,5)	-01	✓
5	1	0	1	(2,3)	01-	✓
6	1	1	0	(2,6)	-10	✓
				(4,5)	10-	✓
				(4,6)	1-0	✓

prime implicant $\bar{b}, \bar{a}, \bar{c}$

Essential prime implicants are $\bar{a}, \bar{b}, \bar{c}$

	0	1	2	3	4	5	6
a	✓	✓	✓	✓			
b	✓	✓			✓	✓	
c	✓		✓		✓	✓	

$$\text{④ } f(a,b,c,d) = \sum_m (0, 2, 3, 4, 8, 10, 12, 13, 14)$$

	a	b	c	d	
0	0	0	0	0	(0,2) 00-0 ✓
2	0	0	1	0	(0,4) 0-00 ✓
4	0	1	0	0	(0,8) -000 ✓
8	1	0	0	0	(Q,3) 001- \bar{ABC}
3	0	0	1	1	(Q,10) -010 ✓
10	1	0	1	0	(4,12) -100 ✓
12	1	1	0	0	(8,10) 10-0 ✓
13	1	1	0	1	(8,12) 1-00 ✓
14	1	1	1	0	(10,14) 1-10 ✓ (12,13) 110- \bar{abc} (12,14) 11-0

Prime implicants $\bar{a}\bar{b}c$, $a\bar{b}\bar{c}$, $\bar{b}\bar{a}$, $\bar{c}\bar{d}$, $a\bar{d}$

Essential prime implicants $\bar{c}\bar{d}$, $a\bar{d}$, $\bar{a}\bar{b}c$, $a\bar{b}\bar{c}$

	0	1	2	3	4	8	10	12	13	14
$\times \bar{b}\bar{d}$	x		x		x	x		x		
$\times \bar{c}\bar{d}$	x			x	x		x		x	
$\times a\bar{d}$					x	x	x			
$\times \bar{a}\bar{b}c$		x	x				x	x		
$\times a\bar{b}\bar{c}$										

$$\Theta f(a,b,c,d) = \sum m (0, 1, 2, 3, 10, 11, 12, 13, 14, 15)$$

	a	b	c	d							
0	0	0	0	0	(0,1)	000-	✓	(0,1)	(2,3)	00--	$\bar{a}\bar{b}$
1	0	0	0	1	(0,2)	00-	0	(0,2)	(1,3)	00-	-
2	0	0	1	0							
3	0	0	1	1	(1,3)	00-1	✓	(2,3)	(10,11)	-01-	$\bar{b}c$
10	1	0	1	0	(2,3)	001-	✓	(2,10)	(3,11)	-01-	-
12	1	1	0	0	(2,10)	-010	✓				
11	1	0	1	1	(3,11)	-011	✓	(10,11)	(14,15)	1-1-	ac
13	1	1	0	1	(10,11)	101-	✓	(10,14)	(11,15)	1-1-	-
14	1	1	1	0	(10,14)	1-10	✓	(12,13)	(14,15)	11--	ab
15	1	1	1	1	(10,14)	110-	✓	(12,14)	(13,15)	11--	-
					(11,15)	1-11	✓				
					(13,15)	11-1	✓				
					(14,15)	111-	-				

Prime implicants $\bar{a}\bar{b}$, $\bar{b}c$, ac , ab

	0	1	2	3	10	11	12	13	14	15	essential PI
$\times \bar{a}\bar{b}$	v	v		v	v						$\bar{a}\bar{b}$
$\times \bar{b}c$			v	v		v	v				ac
$\times ac$							v	v			ab
$\times ab$					x	x	x	x	x	x	

$$\textcircled{2} f(a,b,c,d) = \sum_m (7, 9, 12, 13, 14, 15) + \sum_d (4, 11)$$

	a	b	c	d			
4	0	1	0	0	(4, 12)	-100	$\bar{b}\bar{c}\bar{d}$
9	1	0	0	1	(9, 11)	10-1	$(9, 11)(13, 15)$
12	1	1	0	0	(9, 13)	1-01	$(9, 13)(11, 15)$
7	0	1	1	1	(12, 13)	110-	$(12, 13)(14, 15)$
11	1	0	1	1	(12, 14)	11-0	$(12, 14)(13, 15)$
13	1	1	0	1	(7, 15)	-111	bcd
14	1	1	1	0	(11, 15)	1-11	
15	1	1	1	1	(13, 15)	11-1	
					(14, 15)	111-	

Prime implicants $\bar{b}\bar{c}\bar{d}$, bcd , ad , ab

	7	9	12	13	14	15	H	11
bcd	x				x			
ad		x	x	x	x	x		
ab			x	x	x	x		
$\bar{b}\bar{c}\bar{d}$			x			x		

essential prime implicants are bcd , ad , ab , $\bar{b}\bar{c}\bar{d}$

$$\textcircled{2} f(a,b,c,d) = \sum_m (3, 4, 5, 7, 10, 12, 14, 15) + \sum_d (2)$$

prime implicants $\bar{a}\bar{b}c$, $\bar{b}c\bar{d}$, $\bar{a}b\bar{c}$, $b\bar{c}\bar{d}$

$\bar{a}cd$, $\bar{a}bd$, acd , abd , bcd , abc

Essential PI : $\bar{b}\bar{c}\bar{d}$, $\bar{a}cd$, $\bar{a}bd$, acd , abc
or

$\bar{a}b\bar{c}$, $b\bar{c}\bar{d}$, $\bar{a}cd$, $ac\bar{d}$, bcd

	a	b	c	d	
2	0	0	1	0	✓
4	0	1	0	0	✓
3	0	0	1	1	✓
5	0	1	0	1	✓
10	1	0	1	0	✓
12	1	1	0	0	✓
7	D	1	1	1	✓
14	1	1	1	0	✓
15	1	1	1	1	✓
	(2,3)	0	0	1	-
	(2,10)	-	0	1	0
	(4,5)	0	1	0	-
	(4,12)	-	1	0	0
	(3,7)	0	-	1	1
	(5,7)	0	1	-	1
	(10,14)	1	-	1	0
	(12,14)	1	1	-	0
	(7,15)	-	1	1	1
	(14,15)	1	1	1	-

	3	4	5	7	10	12	14	15
$\bar{a}\bar{b}c$	x							
$\bar{b}c\bar{d}$						x		
$\bar{a}b\bar{c}$		x	x					
$b\bar{c}\bar{d}$		x			x		x	
$\bar{a}cd$	x			x	x			
$\bar{a}bd$			x	x		x	x	
$\bar{a}cd$						x	x	
$\bar{a}b\bar{d}$				x				
$b\bar{c}d$						x	x	x
abc								

⑧ $f(a b c d) = \overline{\prod_M \{ 0, 6, 7, 8, 9, 13 \}}$

$$m_i = \overline{M_i}$$

$$f = M_0 \cdot M_6 \cdot M_7 \cdot M_8 \cdot M_9 \cdot M_{13}$$

$$\overline{f} = \overline{M_0 \cdot M_6 \cdot M_7 \cdot M_8 \cdot M_9 \cdot M_{13}}$$

$$= \overline{m_0} + \overline{m_6} + \overline{m_7} + \overline{m_8} + \overline{m_9} + \overline{m_{13}}$$

$$= m_0 + m_6 + m_7 + m_8 + m_9 + m_{13}$$

	a	b	c	d	
0	0	0	0	0	(0,8) - 000
8	1	0	0	0	(8,9) 100 -
6	0	1	1	0	
9	1	0	0	1	(6,7) 011 -
7	0	1	1	1	(9,13) 1-01
13	1	1	0	1	

Prime implicants are $b+c+d$, $\bar{a}+b+c$, $a+\bar{b}+\bar{c}$
 $\bar{a}+c+\bar{d}$

	0	6	7	8	9	13
$\bar{b}\bar{c}\bar{d}$	x			x		
$\bar{a}\bar{b}\bar{c}$				x	x	
$\bar{a}\bar{b}c$		x	x			
$a\bar{c}d$				x	x	

Essential prime implicants are $b+c+d$, $a+\bar{b}+\bar{c}$
 $\bar{a}+c+\bar{d}$

① $f(a,b,c,d) = \overline{\Pi}_M (0, 6, 7, 8, 9, 13) + \overline{\Pi}_D (5, 15)$

	a	b	c	d	
0	0	0	0	0	(0,8) - 000
8	1	0	0	0	(8,9) 100 -
5	0	1	0	1	(5,7) 100 -
6	0	1	1	0	(5,7) 01-1 ✓
9	1	0	0	1	(5,13) -101 -
7	0	1	1	1	(6,7) 011 -
13	1	1	0	1	(9,13) 1-01
15	1	1	1	1	(7,15) -111 ✓

Prime implicants $b+d$, $b+c+d$, $\bar{a}+b+c$, $a+b+c$
 $\bar{a}+c+\bar{d}$

	0	6	7	8	9	13
$b\bar{d}$			x		x	
$\bar{b}cd$	x			x	x	
$a\bar{b}\bar{c}$			x	x		
$\bar{a}bc$	x	x		x	x	
$a\bar{c}d$						

Essential prime implicants $b+c+d$, $\bar{a}+b+c$, $a+b+c$
 $\bar{a}+c+\bar{d}$

(10) $f(a,b,c,d) = T_M(0,2,3,4,5,12,13) + T_D(8,10)$
 PI - $a+b+\bar{c}$, $b+d$, $c+d$, $\bar{b}+c$ EPI = $a+b+\bar{c}$, $b+d$, $\bar{b}+c$

Hazards & Hazard Covers

Simplification Techniques gives minimal expressions for a logic equation. Simplified equations can be realized using minimum hardware. But TD overcome some practical problems, in certain cases we may prefer to include more terms in the simplified equation. Practical logic circuits do not generate O/P's instantaneously. There is a finite propagation delay. This propagation delay gives rise to several hazards.

Hazard covers are additional terms in a logic equation that prevent hazards. For combinational logic circuits hazards may go unnoticed but in sequential logic circuit it may cause major malfunctioning.

Type of Hazards

Static Hazards

A static hazard occurs if an output signal is supposed to remain at a particular logic value when an input variable changes its value, but instead the signal undergoes a momentary change in its required value.


Static-1 Hazard

This type of hazard occurs when $y = A + A'$ type of situation appears for a logic circuit for certain combination of other inputs & A makes a transition $1 \rightarrow 0$.

An $A + A'$ condition should always generate logic 1 at the output, ie static-1

A	A'	$y = A + A'$
1	0	$1+0=1$
0	1	$0+1=1$

Consider simple logic circuit

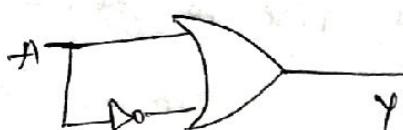


The NOT gate output takes finite time to become logic following $1 \rightarrow 0$ transition at the input A.

The OR gate output goes to logic 0 for a small duration which is unwanted

A	A'	$Y = A + A'$
1	0	$1+0=1$
0	1	$0+1=1$
0	0	$0+0=0$

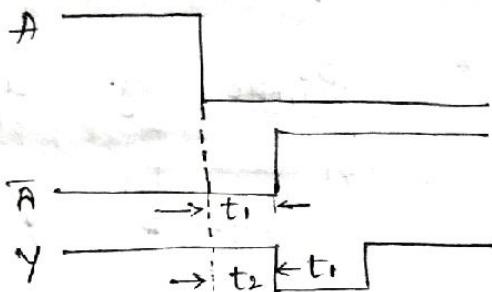The width of this logic o/p is in nanoseconds and called a glitch.




t_1 = NOT gate delay

t_2 = OR gate delay



Static-1 hazard cover

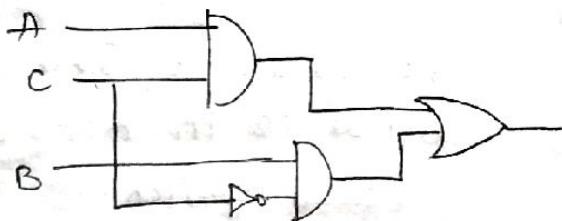Consider $Y = AC + BC'$, corresponding logic circuit



Consider if $A=1, B=1$ & C makes a transition $1 \rightarrow 0$.

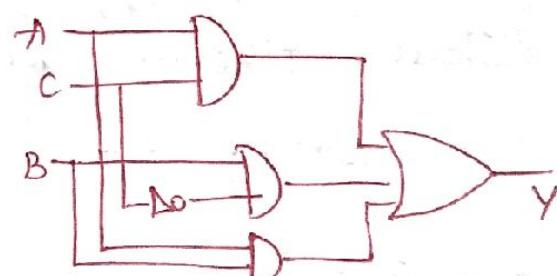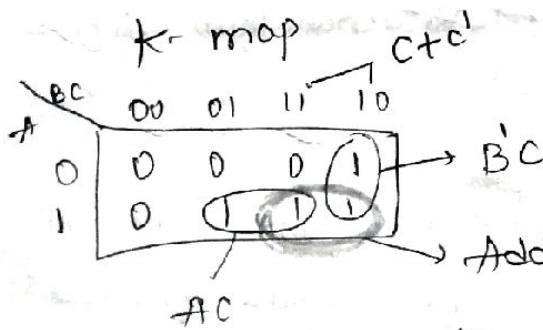the o/p has a glitch & hence the circuit has static-1 hazard.



$$Y = B'C + AC + AB$$


The additional term AB ensured $Y=1$ for $A=1 \& B=1$ & a $1 \rightarrow 0$ transition at C does not affect the o/p

The circuit free from static-1 hazard is shown above.

Static 0 Hazard

This type of hazard occurs when $Y = A \cdot A'$ type of situation appears for a logic circuit for certain combination of other inputs & A makes a transition $0 \rightarrow 1$. An $A \cdot A'$ condition should always generate logic 0 at o/p, i.e. Static 0.


A	A'	$Y = A \cdot A'$
0	1	$0 \cdot 1 = 0$
1	0	$1 \cdot 0 = 0$

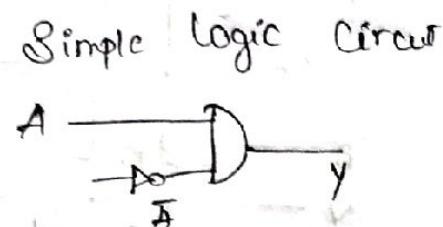

The NOT gate o/p takes finite time to become logic 0 following $0 \rightarrow 1$ transition at the input A. The AND gate output goes to logic 1 for a small duration which is unwanted.


A	A'	$Y = A \cdot A'$
0	1	$0 \cdot 1 = 0$
1	0	$1 \cdot 1 = 1$
1	0	$1 \cdot 0 = 0$

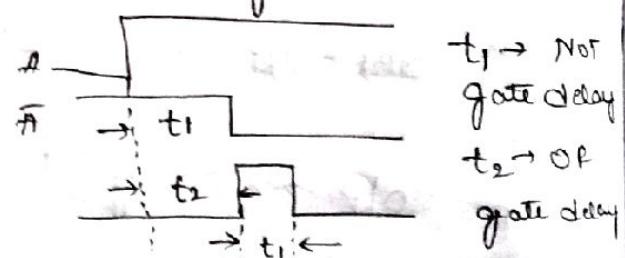The width of this logic 1 output is in nano sec called glitch.



Static 0 hazard cover


$$Y = (B+C) \cdot (A+C')$$

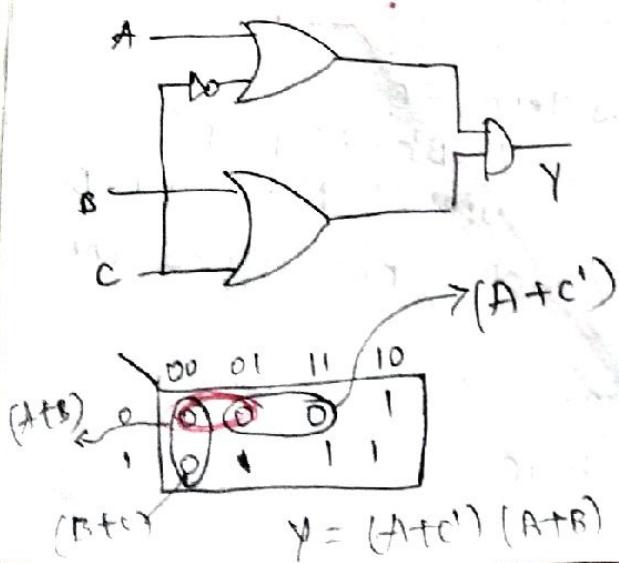

$$Y = (A+C') \cdot (A+B) \cdot (B+C)$$

Additional term $(A+B)$ ensures $Y=0$ for $A=0, B=0$ and $0 \rightarrow 1$ transition at C does not affect the o/p

The hazard free cktr is

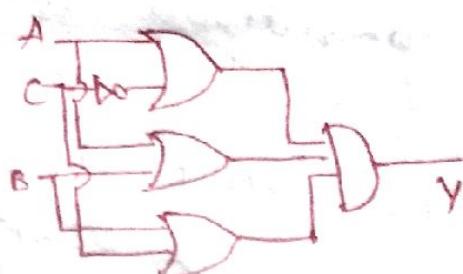

Dynamic hazard

Dynamic hazard cause glitches on $0 \rightarrow 1$ or $1 \rightarrow 0$ transitions of an output signal. When only one transition is required, the output makes multiple transitions.

It is caused by the structure of the logic circuit where there exists multiple paths for a given signal

Change to propagate along:
 $1 \rightarrow 0 \rightarrow 1: 1 \rightarrow 0 \rightarrow 1 \rightarrow 0 \quad Y = A + \bar{A} \cdot A$
 $0 \rightarrow 1 \quad 0 \rightarrow 1 \rightarrow 0 \rightarrow 1 \quad Y = (A + \bar{A}) \cdot A$

Dynamic hazards are encountered in multiple level circuits. They are not easy to detect.

They can be avoided simply by using two level circuits and ensuring that there are no static hazards.

HDL implementation of Combinational

- ✓ Data flow modeling
- ✓ Behavioral modeling

VINUTHA. K M.Tech, (Ph.D.)

Assistant Professor

Dept. of ISE

BMSIT & M. Yelahanka, Bengaluru 56

Table 3.12 A Partial List of Verilog Operator

Relational Operation	Symbol	Bit-wise Operation	Symbol
Less than	<	Bit-wise NOT	\sim
Less than or equal to	\leq	Bit-wise AND	&
Greater than	$>$	Bit-wise OR	
Equal to	$=$	Bit-wise Ex-OR	\wedge
Not equal to	\neq		
Logical Operation (for expressions)	Symbol	Arithmetic Operation	Symbol
Logical NOT	!	Binary addition	+
Logical AND	$\&\&$	Binary subtraction	-
Logical OR	$\ $	Binary multiplication	*
		Binary division	/