

Module -4

Contents:

- i.** Introduction to VHDL
- ii.** VHDL Models for Multiplexers
- iii.** VHDL Modules
- iv.** Set Reset Latch
- V.** Gated Latches
- Vi.** Edge Triggered D Flip-Flop
- Vii.** S R Flip Flop
- Viii .** J K Flip Flop
- ix.** T Flip Flop
- X.** Flip- Flop with additional inputs

Introduction to VHDL:

VHDL stands for VHSIC hardware description language, VHSIC stands for very high speed integrated Circuit. VHDL is general- purpose hardware description language which can be used to describe and simulate the operation of digital circuits. VHDL can describe a digital system at different levels, behavioral, data flow, and structural.

Structure of VHDL program:


VHDL program has two parts, **Entity part** and **Architecture Part**, Entity block is used to declare all input and output signals, architecture block is used to describe the internal operation of the circuit or module.

Syntax of VHDL program:

```
entity entity_name is
    port (inputs; outputs);
end entity_name;
```


```
architecture architecture_name of entity_name is
    signal internal signals;
begin
    statements;
end architecture_name;
```

 Write VHDL program for the circuit shown below.



```
entity two_gates is
    port (A,B,D: in bit; E: out bit);
end two_gates;
architecture gates of two_gates is
    signal C:bit;
begin
    C <= A and B;
    E <= C or D;
end gates;
```

Write a program for Full adder

 

entity FullAdder is

port (X,Y,C_{in} : **in** bit;
C_{out}, Sum: **out** bit);

end FullAdder;

architecture Equations of FullAdder is

begin

Sum <= X **xor** Y **xor** C_{in};

C_{out} <= (X **and** Y) **or** (X **and** C_{in}) **or** (Y **and** C_{in});

end Equations;

Conditional Signal Assignment:


Syntax:

Signal_name <= expression1 **when** condition1

else expression2 **when** condition2

else expression3;

 Write VHDL program for 2 to 1 Multiplexer using conditional signal assignment



entity Mux is

port(I₀, I₁,A: **in** bit; F:**out** bit);

end Mux;

architecture Equations of Mux is


begin

F <= I₀ **when** A='0'

else I₁;

end Equations;

Write VHDL program for ca

 

```

entity Mux is
    port(C,B,D,A,E: in bit; F:out bit);
end Mux;

```

```

architecture Equations of Mux is
begin

```

```

    F<=A when E='1'
      else B when D='1'
      else C;


```

```

end Equations;

```

 Write VHDL program for 4 to 1 Multiplexer using conditional signal assignment



```

entity Mux is
    port(I0, I1,I2,I3,A,B: in bit; F:out bit);
end Mux;

```

```

architecture Equations of Mux is
begin

```

```

    F<=I0 when A&B = "00"
      else I1 when A&B = "01"
      else I2 when A&B = "10"
      else I3;


```

```

end Equations;

```

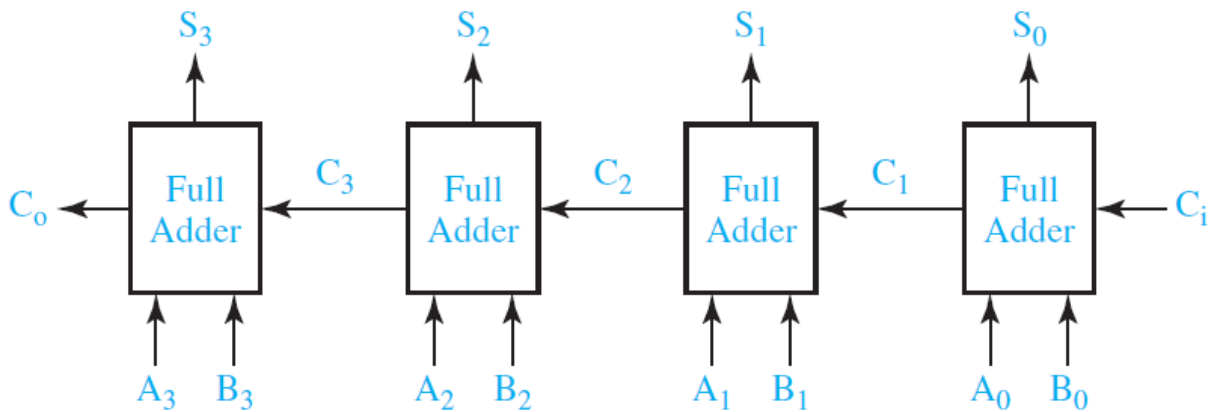Write a VHDL program for 4-bit Binary Adder



In the above circuit, four full adders are used, hence while writing a program we should declare full adder as a component in body of architecture.

entity Adder4 is

port (A, B: **in** bit_vector (3 **downto** 0); C_i : **in** bit;

S: **out** bit_vector(3 **downto** 0); C_o : **out** bit);

End Adder4;

architecture Structure of Adder4 is

component FullAdder

port (X, Y, C_{in} : **in** bit;

C_{out}, Sum : **out** bit);

end component;

begin

FA0: FullAdder **port map** (A(0), B(0), C_i, C(1), S(0));


FA1: FullAdder **port map** (A(1), B(1), C(1), C(2), S(1));

FA2: FullAdder **port map** (A(2), B(2), C(2), C(3), S(2));

FA3: FullAdder **port map** (A(3), B(3), C(3), C_o, S(3));

End Structure;

Set Reset Latch:

 

R	S	Q	Action
0	0	Last state	No change
0	1	1	SET
1	0	0	RESET
1	1	?	Forbidden

In NOR-gate Latch, two NOR gates are used, one of the inputs for NOR gates is S and R respectively, the other two inputs are fed back from the outputs

Case1: When $R=0$ and $S=1$, the output of upper NOR gate is 1 and lower NOR gate output is 0, hence the outputs $Q=1$ $\bar{Q}=0$

Case2: When $R=0$ and $S=0$, the inputs for upper gate are 00 hence the output $Q=1$ and inputs for lower gate are 10 the output $\bar{Q}=0$ (outputs of Flip flop did not change)

Case3: When $R=1$ and $S=0$ the inputs for upper gate are 10 hence the output $Q=0$ and inputs for Lower gate are 00 hence the output $\bar{Q}=1$

Case4: when $R=1$ and $S=1$, the output of both NOR gates become zero, which violates the basic definition of flip flop (\bar{Q} should be complement of Q), hence $R=1$ and $S=1$ input combination is violated in NOR latch


Symbol of SR Latch:




Logic symbol

Gated SR Latch:

Logic Symbol

 

(a) Logic diagram

 

Operation:

- When ENABLE=HIGH, outputs are dependent on R and S, and Latch is said to be enabled.
- When ENABLE=LOW, Latch is disabled, outputs do not change with change in inputs R and S, Latch holds the previous state.


Truth table of Clocked RS Flip-Flop:

EN	S	R	Q_{n+1}
1	0	0	Q_n (no change)
1	0	1	0
1	1	0	1
1	1	1	? (Illegal)
0	X	X	Q_n (no change)



Logic Circuit:



Timing Diagram of Clocked RS Flip-Flop:

 

Gated D Latch

  


Operation:

- When $EN=0$, flip flop is disabled, irrespective of D input, flip flop remains in previous state ($Q=$ Last state)
- When $EN=1$, flip-flop is transparent i.e., output depends on D (when $D=0$ $Q=0$, When $D=1$ $Q=1$)

Truth table of D-Flip-Flop:


EN	D	Q_{n+1}
0	X	Q_n (last state)
1	0	0
1	1	1

Timing Diagram of Clocked D-Flip-Flop:

 


Positive Edge triggered SR Flip-Flop:

Logic Diagram:

 

Symbol:

 

The Clock (c) is applied to positive pulse forming circuit, pos to gated RS Flip-Flop. The small triangle inside the symbol indicates that Q changes during positive edge of the clock.

Operation:

Case 1: When $C=0$, output of both And gates are 0, hence flip-flop output Q_{n+1} =Last state.

Case 2: When $C=1$ $S=0$ $R=1$, output of upper AND gate is 0, and lower AND gate output is 1, hence flip flop output $Q_{n+1}=0$

Case3: When $C=1$ $S=1$ $R=0$, output of upper AND gate is 1, and lower AND gate output is 0, hence flip flop output $Q_{n+1}=1$


Case 4: When $C=1$ $S=1$ $R=1$, output of upper AND gate is 1, and lower AND gate output is 1, hence flip flop output Q_{n+1} =forbidden

Truth Table of Positive Edge-Triggered RS Flip-Flop:

C	S	R	Q_{n+1}	Action
↑	0	0	Q_n	No change
↑	0	1	0	RESET
↑	1	0	1	SET
↑	1	1	?	Illegal

(c) Truth table

 3.20 Positive Edge triggered D-Flip Flop:



D Flip-Flop has only one input (D), when clock $C=0$ the output Q remains in the last state, when Clock C is positive going (\uparrow) output Q depends on D

Case1: when $C=0$, outputs of both AND gates are zero, hence Q_{n+1} remains in the last state

Case 2: When $C=1$, $D=0$, output of upper AND gate $=0$ and output of Lower AND gate $=1$ hence Flip-flop output $Q_{n+1}=0$


Case3: When $C=1$, $D=1$, output of upper AND gate $=1$ and output of Lower AND gate $=0$, hence Flip-flop output $Q_{n+1}=1$

Truth table of positive-Edge Triggered D-Flip Flop:


C	D	Q_{n+1}
0	X	Q_n (last state)
\uparrow	0	0
\uparrow	1	1

(c) Truth table

Symbol

 

 3.21 Positive Edge Triggered JK flip Flop:



In Positive-Edge Triggered JK Flip-Flop, inputs are J and K the output Q is fed back to the Lower AND gate, and output \bar{Q} is fed back to upper AND gate.

Operation:

Case1: when $C=0$, outputs of both AND gates are 0 hence, the output Q_{n+1} remains in last state.

Case2: When C is 1, $J=0$ $K=0$ both AND gate outputs are 0, hence Flip flop output Q_{n+1} remains in last state Q_n

Case3: When C is 1, $J=0$ $K=1$, $Q_n=1$ upper AND gate output is zero and Lower AND gate output is 1, hence Flip flop output Q_{n+1} is 0


Case4: When C is 1, $J=1$ $K=0$, $Q_n=0$ upper AND gate output is 1 and Lower AND gate output is 0, hence Flip flop output Q_{n+1} is 1

Case 5: When $C=1$, $J=1$, $K=1$ the output $Q_{n+1}=\bar{Q}_n$ (outputs Toggle)

Truth Table of Positive Edge triggered JK Flip-Flop:

C	J	K	Q_{n+1}	Action
↑	0	0	Q_n (last state)	No change
↑	0	1	0	RESET
↑	1	0	1	SET
↑	1	1	\bar{Q}_n (toggle)	Toggle


Symbol:

 

T Flip-Flop:

- T Flip-Flop is also called as Toggle Flip-Flop.
- T Flip-Flop has only one input.

Symbol:

 


Truth Table:


CLK	T	Q_{n+1}
0	x	Q_n
↑	0	Q_n
↑	1	$\overline{Q_n}$

Flip-Flop with additional Inputs:

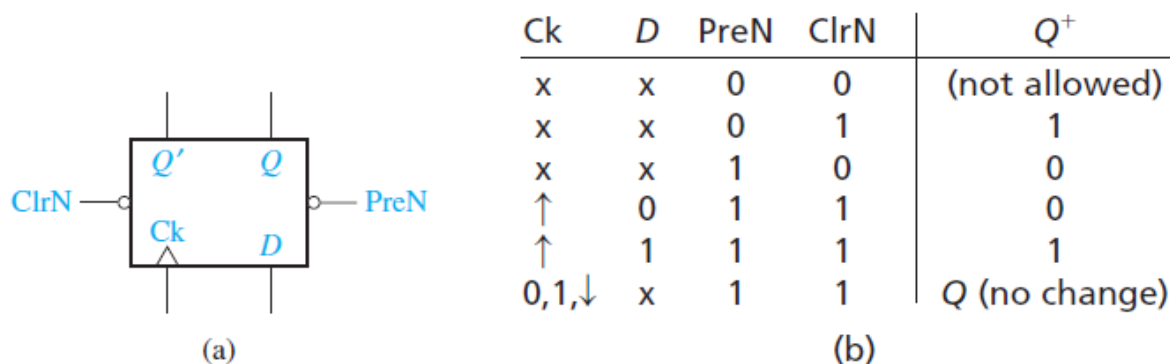In a Flip-Flop, **preset** and **clear** inputs are additional inputs, these inputs are also called as asynchronous inputs since their operation does not depend on the clock.




As shown in the above figure, the small circles on the inputs preN and clrN indicate that a logic 0 is required to clear or set the flip-flop, this type of inputs is often referred to as **active-low** inputs because a low voltage or logic 0 will activate the clear or preset inputs. A logic 0 applied to clear will reset the flip flop to $Q=0$ and a 0 applied to preset will set the flip flop to $Q=1$.

 

The above timing diagram depicts the operation of clear and preset inputs, at time t_1 , $\text{clrN}=0$ holds the Q output at 0, so the rising edge of the clock is ignored, At t_2 and t_3 normal state changes occur because clrN and preN are both 1, then Q is set to 1 by $\text{preN}=0$ but Q is cleared at t_4 by the rising edge of the clock because $D=0$ at that time.

JK Master Slave Flip- Flop:

 

- Two flip-flops are used in JK master Slave Flip-Flop, first Flip-Flop is **Master**, Second Flip-Flop is **Slave**, Master is Positive Level-triggered Flip-Flop and Slave is Negative Level-Triggered Flip-Flop. Output of Master Flip flop is depends on inputs J and K when Clock is positive, output of master is connected to Slave, hence Slave follows the Master when clock is negative.


Case 1: when clock $C=1$, and inputs $J=K=0$, master output remains in last state, slave follows the master when $C=0$, hence output Q remains in last state

Case2: When $C=1$, $J=1$ and $K=0$, master output is 1, slave follows the master when clock =0, hence $Q=1$

Case 3: when $C=1$, $J=0$, $K=1$ master output is 0, J and K inputs of slave are 0 and 1, when $C=0$, output of slave $Q=0$

Case 4: When $C=1$ $J=1$, $K=1$, Master Toggles, slave also toggles when clock goes Low

Symbol

 


Truth Table:

C	J	K	Q_{n+1}	Action
\neg	L	L	Q_n	No change
\neg	L	H	L	RESET
\neg	H	L	H	SET
\neg	H	H	\bar{Q}_n	Toggle

The symbol \neg appearing next to Q indicates Postponed Output. The master output is dependent on inputs J and K while clock is high, the state of master is shifted to slave when clock goes Low.

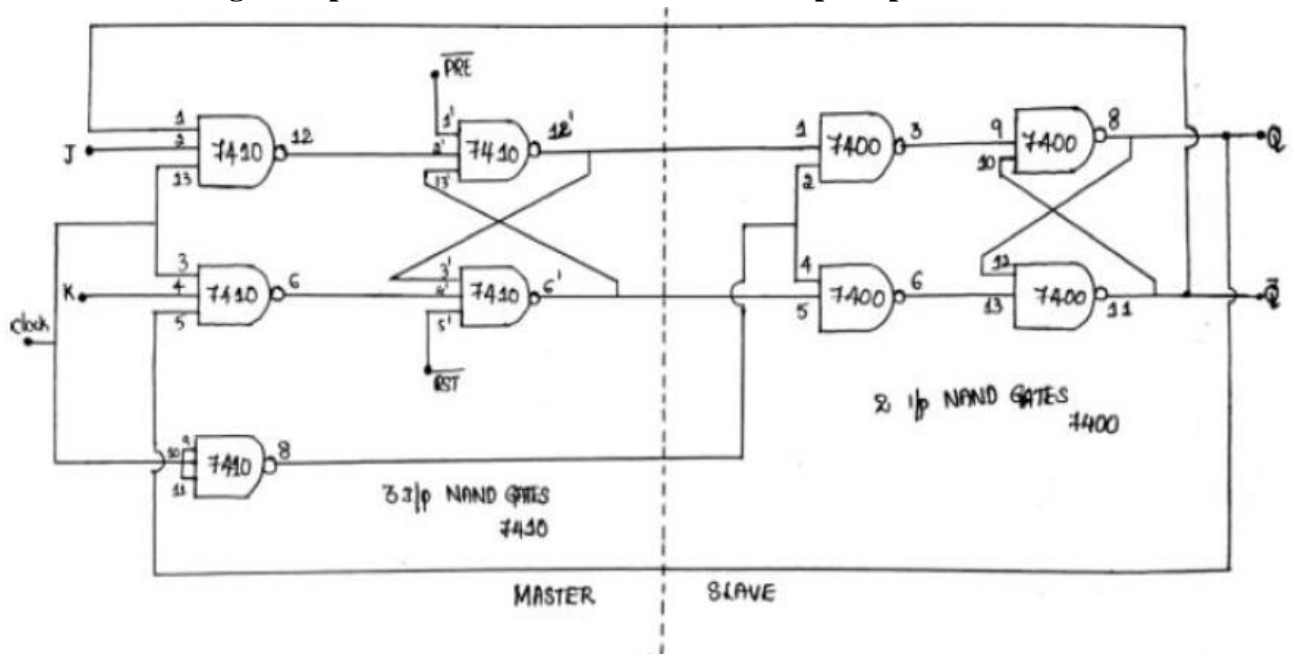Draw NAND-NAND gate implementation of JK master slave Flip-Flop



Important Questions

1. Write VHDL program for 4 to 1 Multiplexer using conditional signal assignment.
2. Write a VHDL program for 4-bit Binary Adder.
3. Explain working principle of gated SR Latch.
4. With circuit diagram and truth table, explain the working of positive edge triggered JK Flip-Flop.
5. Explain working principle of D flip-flop.
6. Define Race-Around condition in JK flip-flop
In JK Flip-flop, when $J=1$ and $K=1$ and clock is positive edge output Q and Qb toggle, this phenomenon is called as Race around condition.
7. Briefly explain about additional inputs of flip-flop with timing diagram.
8. Explain JK master slave flip flop and draw Nand-Nand gate implementation of JK master slave flip-flop.